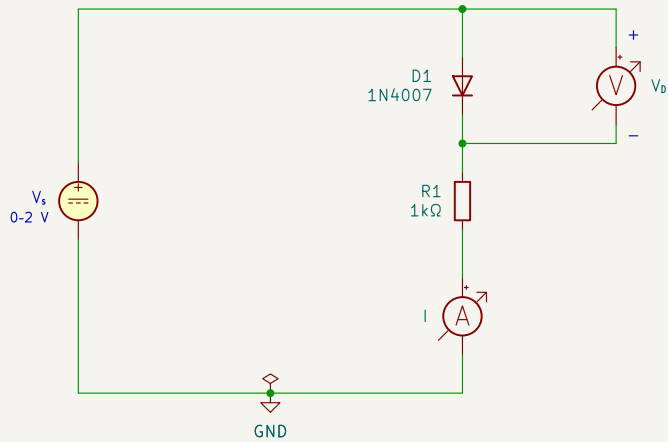


## Lab 1 實驗一：順偏導通電壓量測電路



$$V_s = V_D + I \cdot 1 \text{ k}\Omega$$

### NoteCraft 電子學實作系列

Sheet: /

File: lab1-exp1-forward.kicad\_sch

**Title: Lab 1 實驗一：順偏導通電壓**

Size: A5

Date: 2026-09-19

Rev: 1

KiCad E.D.A. 10.0.6

Id: 1/1